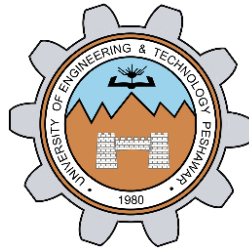


Lab Report - 10

BJT BIASING CIRCUITS Voltage-Divider-Bias Configuration



Spring-24

CSE-206L Electronics Circuits Lab

Submitted by: **Hassan Zaib Jadoon**

Registration No: **22PWCSE2144**

Section: **A**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Submitted to:

Engr. Usman Malik

Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar

Objectives:

To determine the quiescent operating conditions of the fixed-bias BJT configuration.

Components:

- Resistors: 680Ω, 1.8 kΩ, 6.8 kΩ, 33 kΩ
- Transistors: 2N3904, 2N4401
- DC Power Supply
- DC Ammeter
- DC Voltmeter

Procedure:

1. Measure all resistor values (R1, R2, RB and RC) from circuit in Fig. 1
2. Using the β determined for 2N3904 transistor in Part B, calculate the theoretical values of V_B , V_E , I_E , I_C , V_C , V_{CE} and I_B for the network shown in Fig. 1. Record them in Table
3. Construct the network of Fig. 1 and measure V_B , V_E , V_C and V_{CE} . Record them in Table.

Transistor 2N3904:

$$I_B = 1.22\text{mA}$$

$$I_C = 4.85\text{mA}$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$V_{CE} = 20 - 0.00485\text{A}(1800 + 680)$$

$$V_{CE} = 7.972\text{ V}$$

$$\beta = \frac{I_C}{I_B}$$

$$\beta = \frac{4.85}{1.22} = 3.975$$


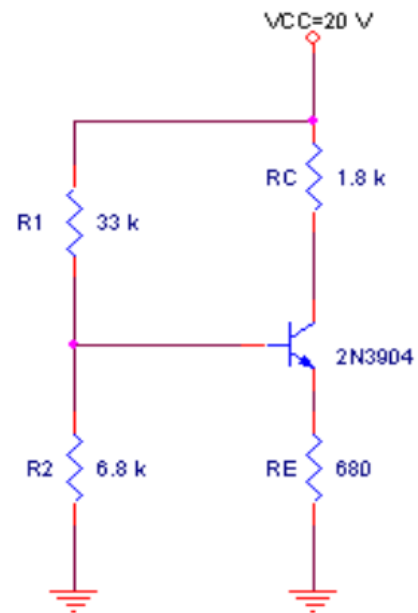


Fig-1

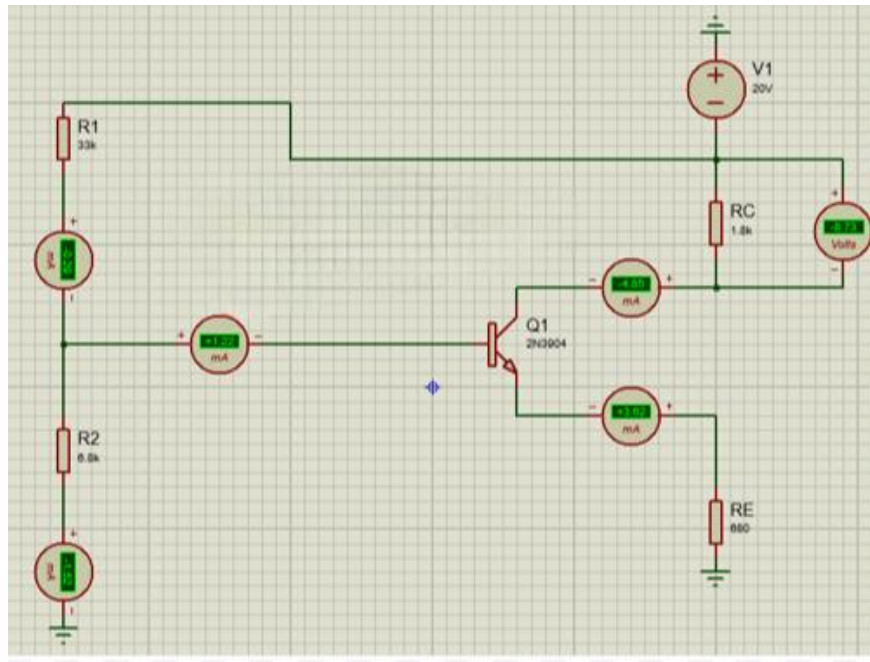

Transistor 2N2222:

$$I_B = 1.22\text{mA}$$

$$I_C = 4.88\text{mA}$$


$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$V_{CE} = 20 - 0.00488(1800 + 680)$$

$$V_{CE} = 7.897\text{V}$$

$$\beta = \frac{I_C}{I_B}$$
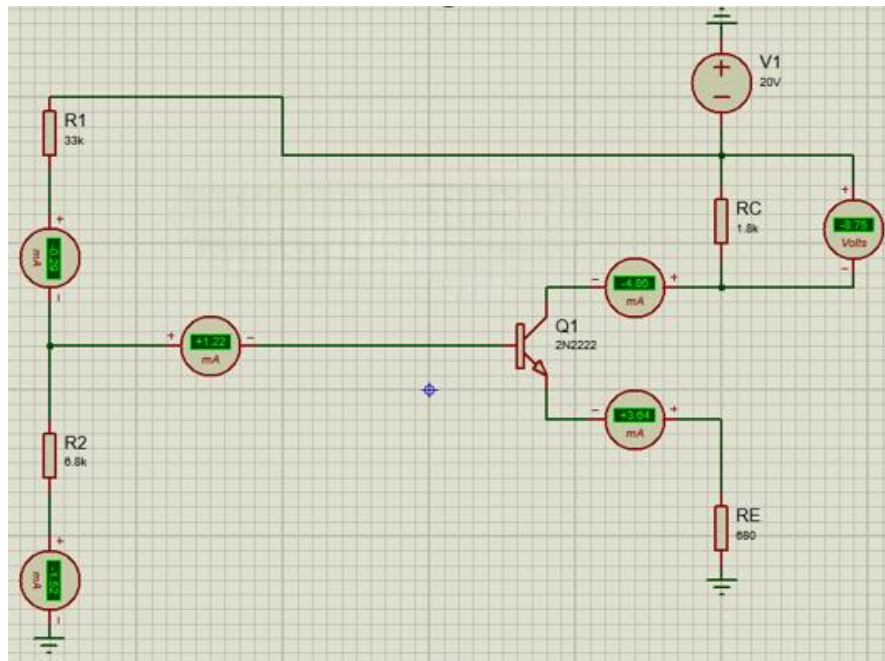
$$\beta = \frac{4.88\text{mA}}{1.22\text{mA}} = 4$$



% Changes:

$$\% \Delta \beta = \frac{|\beta_{2N2222} - \beta_{2N3904}|}{|\beta_{2N3904}|} \times 100 \Rightarrow \frac{4 - 3.97}{3.97} \times 100$$

$$\% \Delta \beta = 0.75\%$$

$$\% I_C = \frac{|I_{C(2222)} - I_{C(3904)}|}{|I_{C(3904)}|} \times 100 \Rightarrow \frac{4.88 - 4.85}{4.85} \times 100$$

$$\% I_C = 0.61\%$$

$$\% V_{CE} = \frac{|V_{CE(2222)} - V_{CE(3904)}|}{|V_{CE(3904)}|} \times 100 \Rightarrow \frac{7.897 - 7.972}{7.972} \times 100$$

$$\% V_{CE} = 0.94\%$$